

# VLSI Design

## Lecture 16: Clocking disciplines


Shaahin Hessabi

Department of Computer Engineering

Sharif University of Technology


Adapted, with modifications, from lecture notes prepared by the  
book's author (from Prentice Hall PTR)

# Flip-flop-based sequential machines

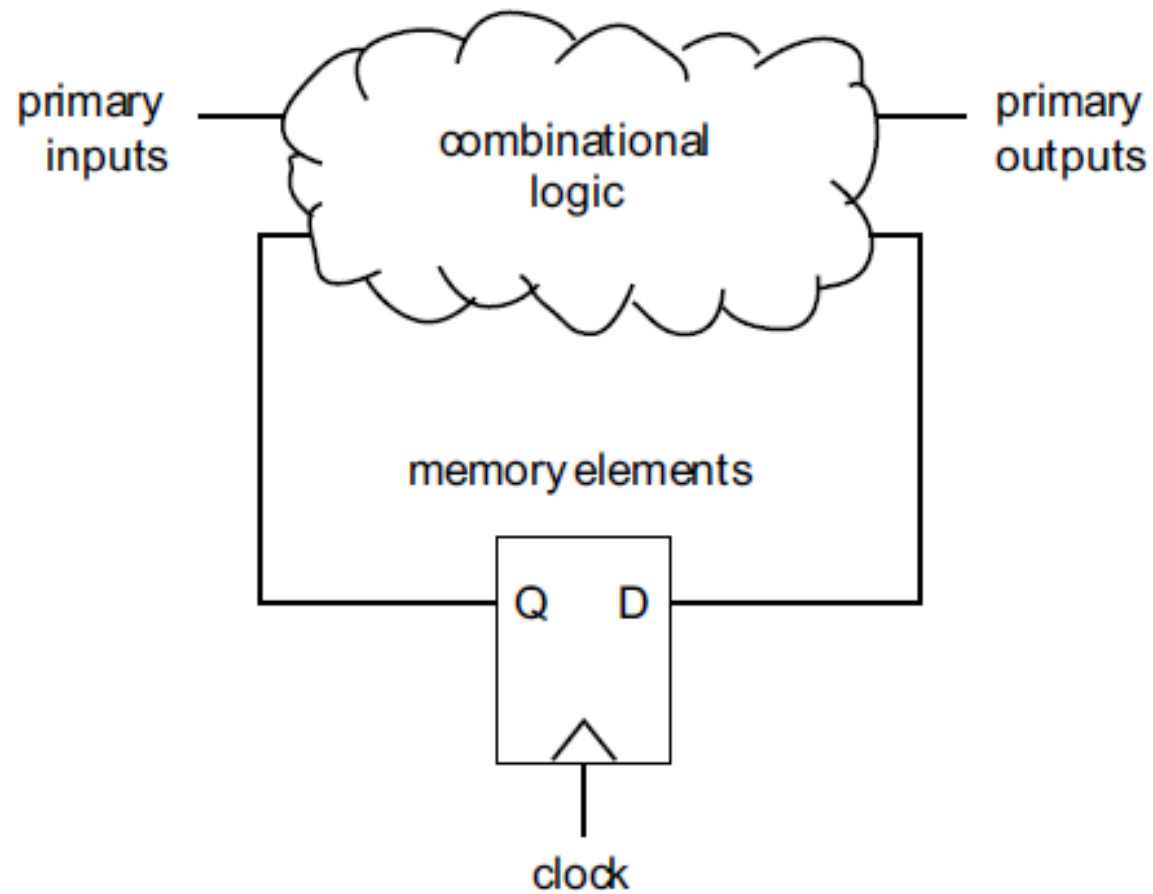
 
# Flip-flop rules

- ❑ Inputs change after clock ( $\phi$ ) edge.
- ❑ Inputs must stabilize before next clock edge.
- ❑ Rules allow changes to propagate through combinational logic for next cycle.
- ❑ Flip-flop outputs hold current-state values for next-state computation.



# Latch-based machines


- ❑ Latches do not cut combinational logic when clock is active.
- ❑ Latch-based machines must use multiple ranks of latches.
- ❑ Multiple ranks require multiple phases of clock.

# Two-sided latch constraint

- ❑ Latch must be open less than the shortest combinational delay.
- ❑ Period between latching operations must be longer than the longest combinational delay.
- ❑ Note: difference between shortest and longest combinational delay may be large ( $\text{sum}_0$  vs.  $\text{sum}_{31}$ ).

# Latch shoot-through


Latch may allow data to shoot through:

 

# Strict two-phase clocking discipline

- ❑ Strict two-phase discipline is conservative but works.
- ❑ Can be relaxed later with proper knowledge of constraints.
- ❑ Strict two-phase machine makes latch-based machine behave more like flip-flop design, but requires multiple phases.

# Strict two-phase architecture

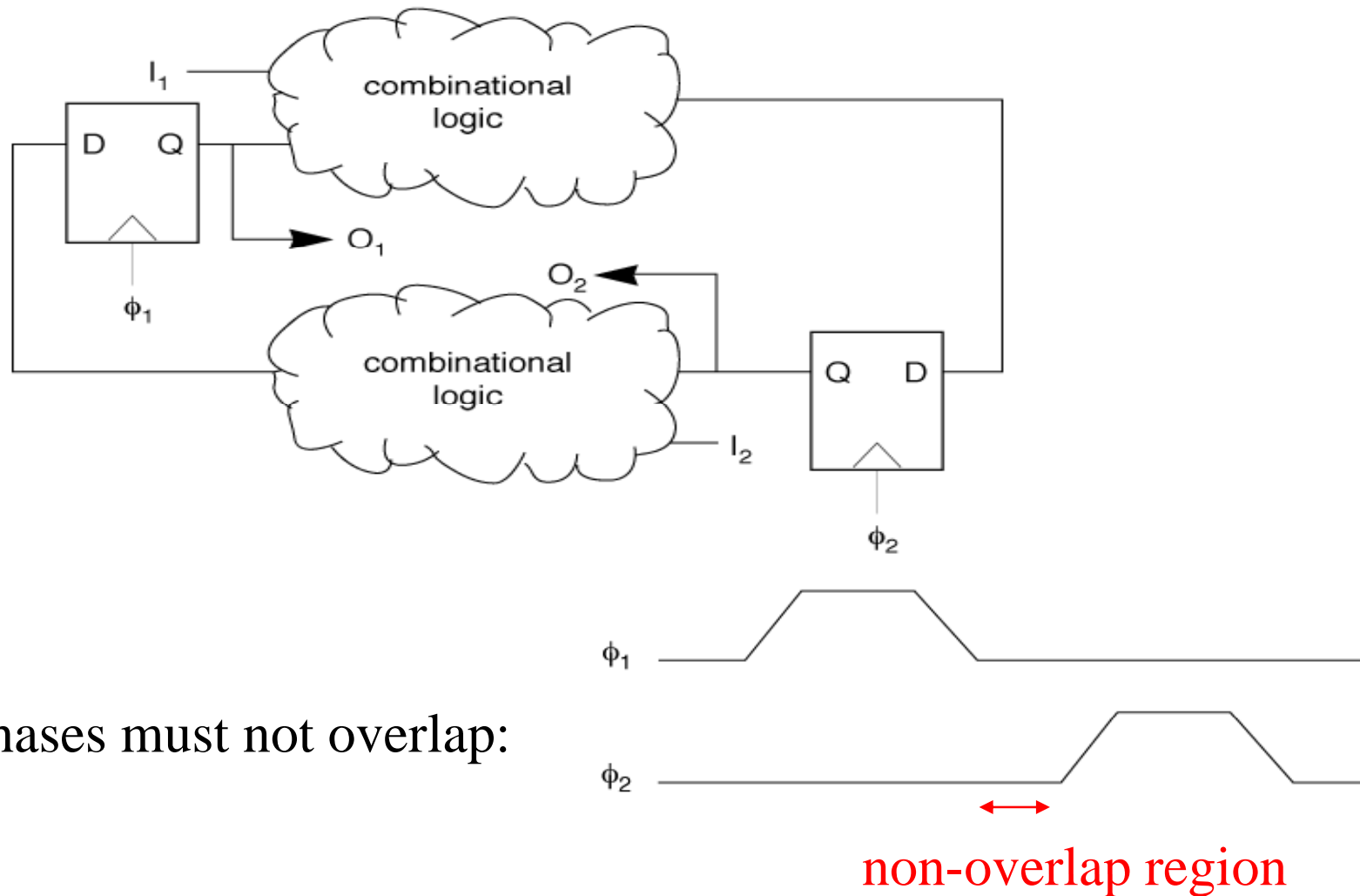




# Why it works

- ❑ Each phase has a **one-sided** constraint: phase must be long enough for all combinational delays.
- ❑ If there are no combinational loops, phases can always be stretched to make that section of the machine work.
- ❑ Total clock period depends on sum of phase periods.
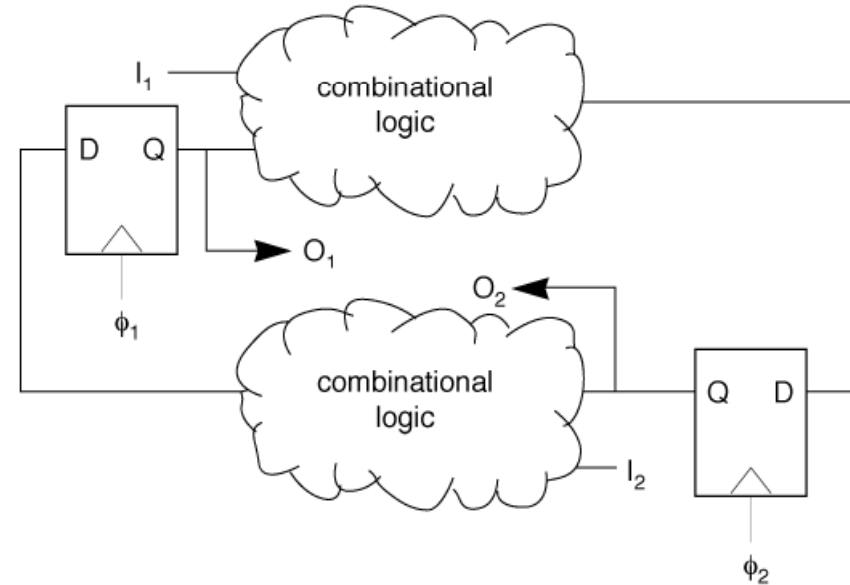
# Clocking types

- ❑ Logic on different phases operate at different times: can't mix signals from different phases.
- ❑ Primary inputs must obey the same rules as internal signals.
- ❑ Clocking types are bookkeeping that help us ensure that machine structure is valid.




# Stable signals

- ❑ A logic signal is always stable during one phase: phase in which the latch which produced it is not active.
- ❑ Easiest to think of machine behavior in terms of stable signals, though signals propagate while not stable.


# Signal types

- Clocks are separate types:  $\phi_1$  ,  $\phi_2$ .
- Two types of stable data signal:
  - ❖ stable  $\phi_1$  (s  $\phi_1$ )
  - ❖ stable  $\phi_2$  (s  $\phi_2$ )
- A stable signal has a complementary valid signal:
  - ❖ stable  $\phi_2$  (s  $\phi_2$ ) = valid  $\phi_1$  (v  $\phi_1$ )

# Stable data signal

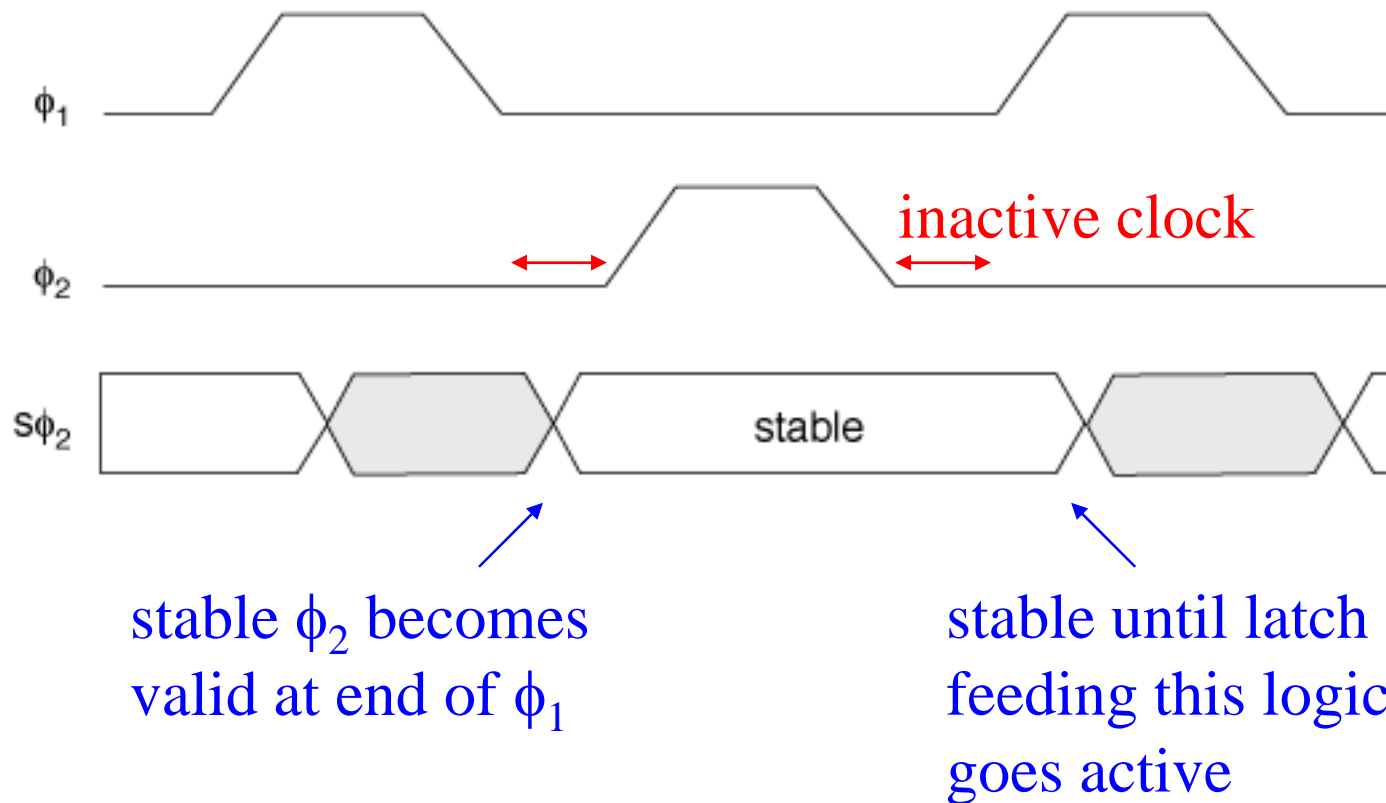


# How clocking types combine

 

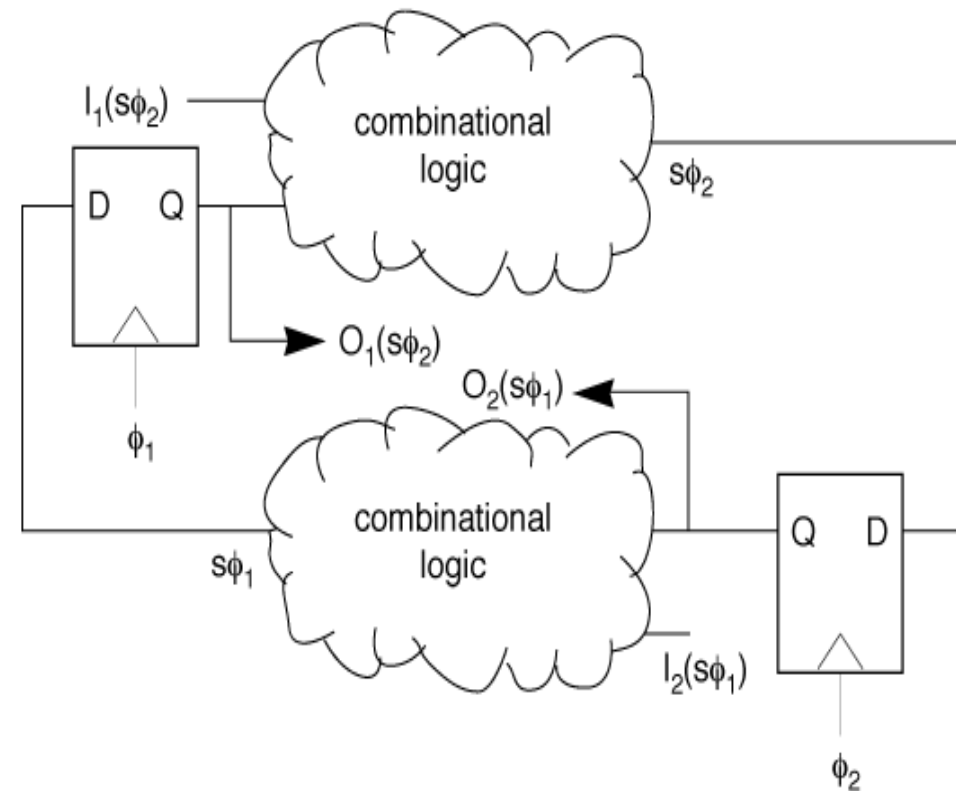
# Clocking types in the two-phase machine

- ❑ Combinational logic does not change type of signal.
- ❑ Primary inputs must be compatible.
- ❑ Latches change signals from one clock type to another.
- ❑ In strict system, never mix clocks with data signals in combinational logic.




# Two-coloring

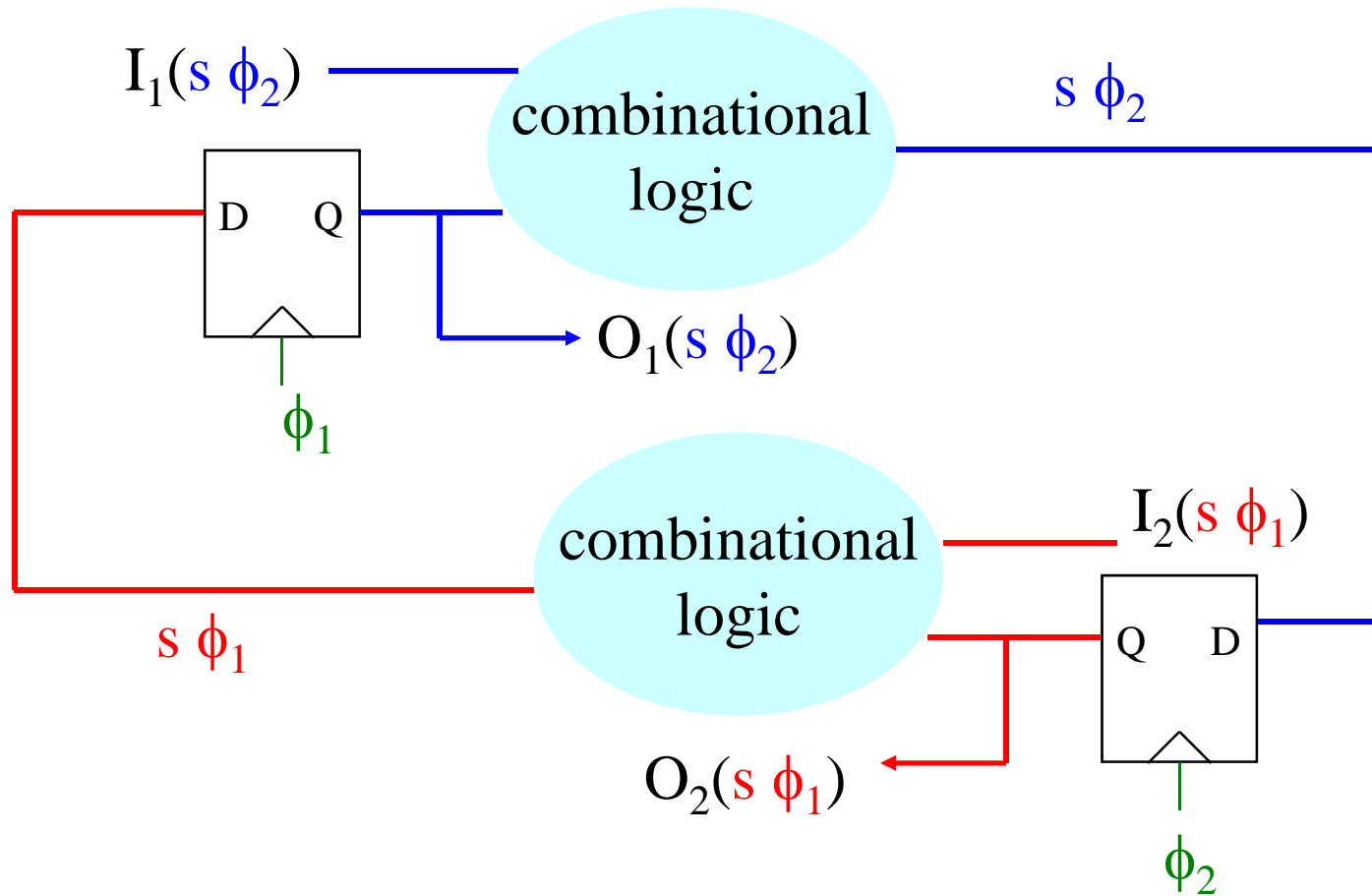



 
# Example: shift register

- Want to displace bit by n registers in n cycles.
- Each register requires two phases:




# Shift register layout

Forms a linear array:

 

# Shift register operation

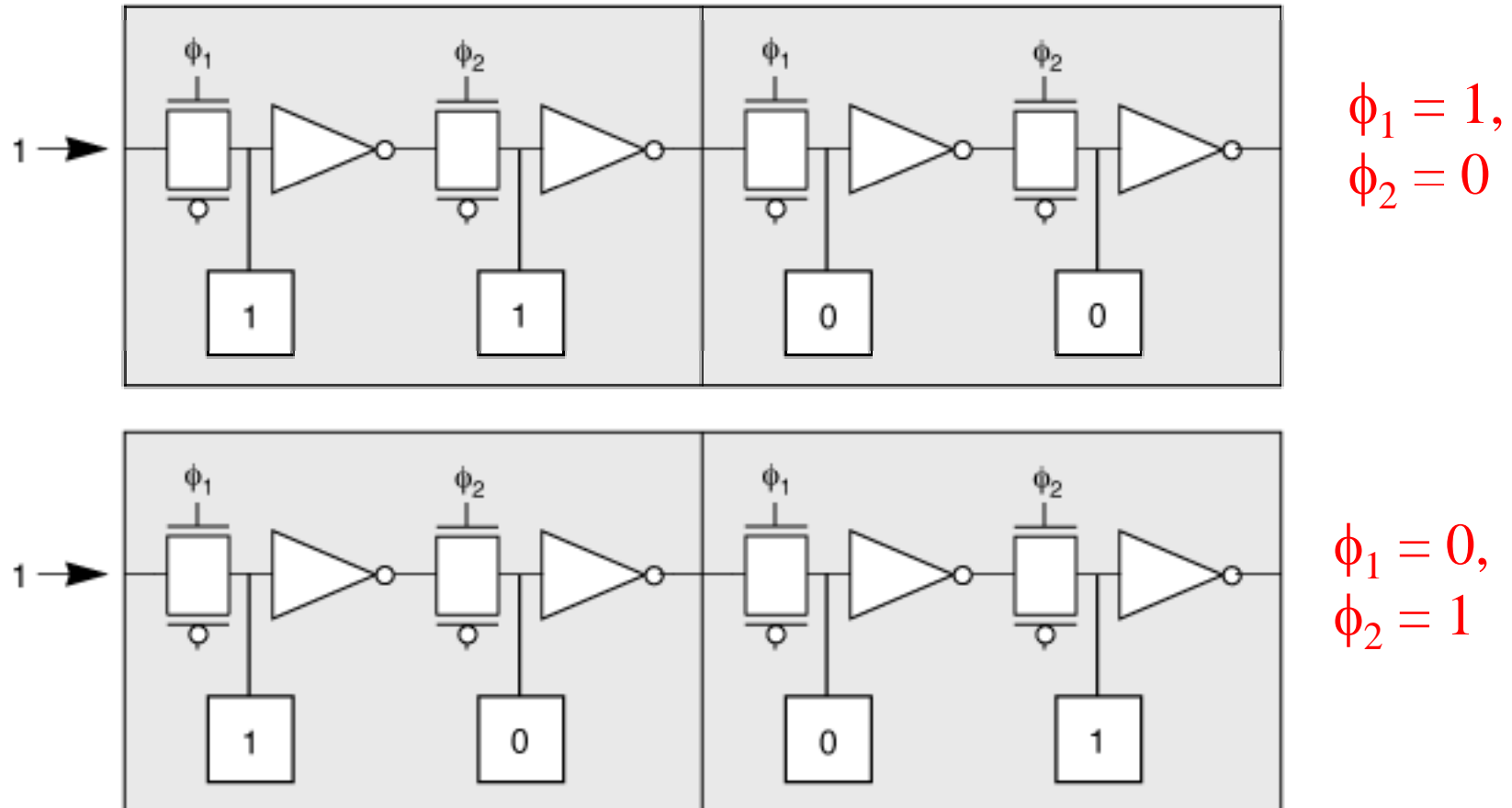

# Non-strict disciplines

- Some relaxation of the rules can be useful:
  - ❖ reduce area;
  - ❖ increase performance.
- Rules must be relaxed in a way that ensures the machine will still work.


# Qualified clocks

- ❑ Use logic to generate a clock signal which is not always active.
- ❑ Qualification must not introduce glitches into the clock: glitches violate the fundamental definition of a clock by introducing extra edges.
- ❑ Use stable signals to qualify clocks.

# Uses of qualified clocks

- ❑ May want to conditionally load a register.
- ❑ May qualify a clock to turn off machine for low-power operation.
- ❑ Latch must keep its value during inactive period.
- ❑ Difficult to ensure that logic value will come high in time: use quasi-static latch.

# Recirculating latch

 

Synchronous design ensures that the system works, in spite of relaxation of the rules.

# Qualified clocks and skew

- ❑ Logic in the clocking path introduces delay.
- ❑ Delay can cause clock to arrive at latches at different times, violating clocking assumptions.
- ❑ When designing qualification logic:
  - ❖ minimize and check skew;
  - ❖ sharpen clock edge.



# Qualification skew example

